

به نام خدا



UNIVERSITY OF TEHRAN
Electrical and Computer Engineering Department

Computer Assignment 3

Digital Systems I - ECE 894

Deadline : 25 Ordibehesht 1400

Erfan Panahi

810198369

Spring 1400

List of Problems:

Computer Assignment 2

Problem 1. Page 2 ([Link](#))

Problem 2. Page 6 ([Link](#))

Problem 3. Page 7 ([Link](#))

Problem 4. Page 8 ([Link](#))

Problem 5. Page 10 ([Link](#))


Problem 6. Page 11 ([Link](#))

Problem 7. Page 12 ([Link](#))

Problem 1. File: Fadder_P1.sv and Fadder_P1_TB.sv

 
A. Circuit diagram:


In following figure we show the design of a full-adder using basic gate structure:



We have used XOR and NAND gates in this structure. So, we show the transistor level structure of this gates.

NAND gate structure:

 

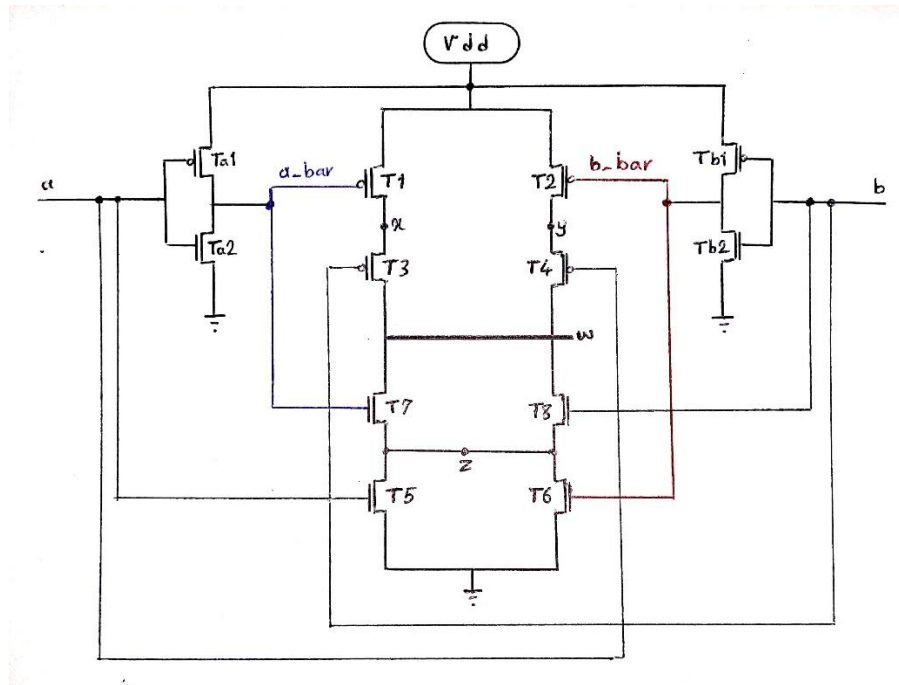XOR gate structure:**B. Worst-cases:****NAND gate :**

We have calculated the worst case of the NAND gate in CA1:

Worst case **To1 : 10NS** ($ab = 11 \rightarrow 10$)

Worst case **To0 : 8NS** ($ab = 10 \rightarrow 11$)

Using 'nand' statement:

```
nand #(10,8) (w,a,b);
```

XOR gate :

We have calculated the worst case of the NAND gate in HW2:

Worst case **To1 : 17NS** ($ab = 11 \rightarrow 10$)

Worst case **To0 : 19NS** ($ab = 10 \rightarrow 11$)

Using 'assign' statement: (Because SystemVerilog does not have XOR statement)

```
assign #(17,19) w = a ^ b;
```

Full-adder :

For So (Sum Out):

Worst case **To1 : 19 + 17 = 36NS** ($abc_i = 101 \rightarrow 001$)

Worst case **To0 : 17 + 19 = 36NS** ($abc_i = 001 \rightarrow 101$)

For Co (Carry Out):

Worst case **To1**: $17 + 8 + 10 = 35\text{NS}$ ($abc_i = 001 \rightarrow 101$)

Worst case **To0**: $19 + 10 + 8 = 37\text{NS}$ ($abc_i = 101 \rightarrow 001$)

c. System Verilog Description:


File: Fadder_P1.sv

```
`timescale 1ns/1ns
module Fadder_P1(input a,b,ci,output so,co);
    wire si,x,y;
    assign #(17,19) si = a ^ b;
    assign #(17,19) so = si ^ ci;
    nand #(10,8) (x,a,b);
    nand #(10,8) (y,si,ci);
    nand #(10,8) (co,x,y);
endmodule
```

File: Fadder_P1_TB.sv

```
`timescale 1ns/1ns
module Fadder_P1_TB();
    logic aa=0,bb=0,cii=0;
    wire soo,coo;
    Fadder_P1 UUT(aa,bb,cii,soo,coo);
    initial begin
        #100 aa = 1;
        #100 bb = 1;
        #100 bb = 0;
        #100 aa = 0;
        #100 cii = 1;
        #100 aa = 1;
        #100 aa = 0;
        #100 $stop;
    end
endmodule
```



d. Image of project and compiling:

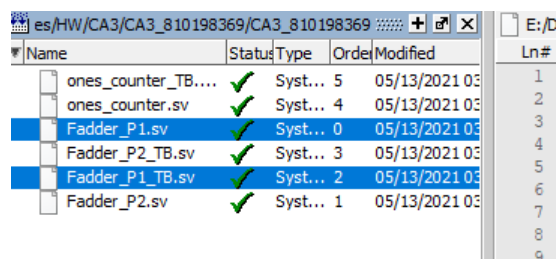



Name	Status	Type	Order	Modified	Ln#
ones_counter_TB....	✓	Syst...	5	05/13/2021 03	1
ones_counter.sv	✓	Syst...	4	05/13/2021 03	2
Fadder_P1.sv	✓	Syst...	0	05/13/2021 03	3
Fadder_P2_TB.sv	✓	Syst...	3	05/13/2021 03	4
Fadder_P1_TB.sv	✓	Syst...	2	05/13/2021 03	5
Fadder_P2.sv	✓	Syst...	1	05/13/2021 03	6
					7
					8
					9

E. Waveform:

Carry Out worst-case:

  


Sum Out worst-case:

  

Problem 2. Files: Fadder_P2.sv

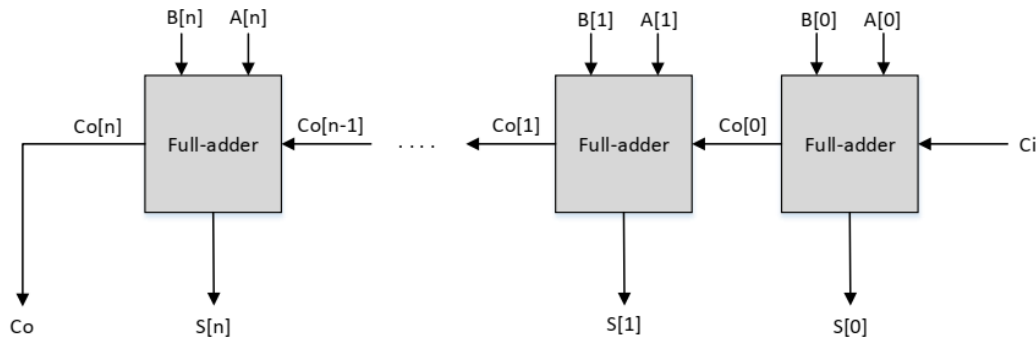A. Delay values and circuit diagram:

According to the Problem 2 of CA for the delay value we assume the adder is realized as a Ripple-carry adder. The diagram of RCA is shown here:



We consider the same worst delay for the both output that is maximum of $T_{01}:\{36,37\}$ $T_{01}:\{36,35\}$. So we can say the worst case delay of the full-adder RTL is:

$$T_{01} = 37NS$$

$$T_{00} = 36NS$$

Using 'assign' statement we write a full-adder:


```
assign #(37,36) {co,so} = a + b + ci;
```

B. System Verilog Description:

File: Fadder_P2.sv

```
`timescale 1ns/1ns
module Fadder_P2 #(parameter n) (input [n-1:0]A,B,input Ci,output [n-1:0]So,output Co);
    assign #(n*37,n*36) {Co,So} = A + B + Ci;
endmodule
```

c. Image of project and compiling:

 

Problem 3. Files: Fadder_P2_TB.sv

A. System Verilog Description:


File: Fadder_P2_TB.sv

```
`timescale 1ns/1ns
module Fadder_P2_TB();
    logic [3:0]AA,BB;
    logic Cii = 0;
    wire [3:0]Soo;
    logic Co;
    Fadder_P2 #4 UUT(AA,BB,Cii,Soo,Co);
    initial begin
        repeat (10) #200 {AA,BB} = $random;
        #200 $stop;
    end
endmodule
```

B. Image of project and compiling:

Name	Status	Type	Order	Modified	Ln#
ones_counter_TB....	✓	Syst...	5	05/13/2021 03	1
ones_counter.sv	✓	Syst...	4	05/13/2021 03	2
Fadder_P1.sv	✓	Syst...	0	05/13/2021 03	3
Fadder_P2_TB.sv	✓	Syst...	3	05/13/2021 04	4
Fadder_P1_TB.sv	✓	Syst...	2	05/13/2021 03	5
Fadder_P2.sv	✓	Syst...	1	05/13/2021 04	6


c. Waveform:

 

Problem 4. Files: My1s_counter.sv

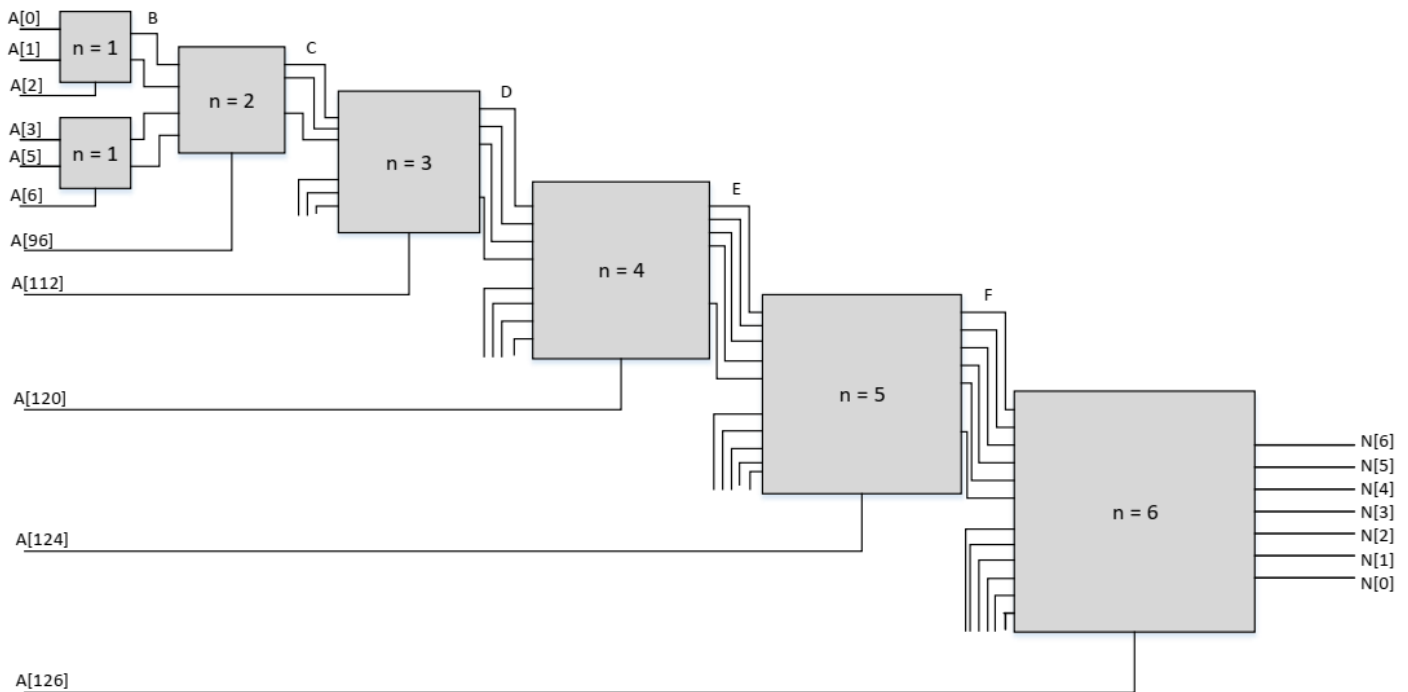A. Circuit diagram:

In following figure we show the design of a 127-bit 1's counter: (It is not complete diagram and each block shows a full-adder.)



B. Worst-case:

As we see we use $n = 1$ -to- 6 full-adders in this RTL. According to Problem 2s' delay we can say:

Worst case of 127 bit 1's counter: $(1 + 2 + 3 + 4 + 5 + 6) \times 37 = 777NS$

c. System Verilog Description:

File: My1s_counter.sv

```
`timescale 1ns/1ns
module My1s_counter127(input [126:0]A,output [6:0]N);
    wire [63:0]B;
    wire [47:0]C;
    wire [31:0]D;
    wire [19:0]E;
    wire [11:0]F;
    genvar i;
    generate
```

```

    for (i=0;i<32;i=i+1) begin: Fa1bit
        Fadder #1 fa1(A[3*i+1],A[3*i],A[3*i+2],B[2*i],B[2*i+1]);
    end
    for (i=0;i<16;i=i+1) begin: Fa2bit
        Fadder #2
fa2({B[4*i+3],B[4*i+2]},{B[4*i+1],B[4*i]},{A[96+i],{C[3*i+1],C[3*i]},{C[3*i+2]};
    end
    for (i=0;i<8;i=i+1) begin: Fa3bit
        Fadder #3
fa3({C[6*i+5],C[6*i+4],C[6*i+3]},{C[6*i+2],C[6*i+1],C[6*i]},{A[112+i],{D[4*i+2],D[4*i+1],D
[4*i]},{D[4*i+3]};
    end
    for (i=0;i<4;i=i+1) begin: Fa4bit
        Fadder #4
fa4({D[8*i+7],D[8*i+6],D[8*i+5],D[8*i+4]},{D[8*i+3],D[4*i+2],D[8*i+1],D[8*i]},{A[120+i],{E
[5*i+3],E[5*i+2],E[5*i+1],E[5*i]},{E[5*i+4]};
    end
    for (i=0;i<2;i=i+1) begin: Fa5bit
        Fadder #5
fa5({E[10*i+9],E[10*i+8],E[10*i+7],E[10*i+6],E[10*i+5]},{E[10*i+4],E[10*i+3],E[10*i+2],E[
10*i+1],E[10*i]},{A[124+i],{F[6*i+4],F[6*i+3],F[6*i+2],F[6*i+1],F[6*i]},{F[6*i+5]};
    end
    for (i=0;i<1;i=i+1) begin: Fa6bit
        Fadder #6
fa6({F[12*i+11],F[12*i+10],F[12*i+9],F[12*i+8],F[12*i+7],F[12*i+6]},{F[12*i+5],F[12*i+4],
F[12*i+3],F[12*i+2],F[12*i+1],F[12*i]},{A[126+i],{N[7*i+5],N[7*i+4],N[7*i+3],N[7*i+2],N[7*
i+1],N[7*i]},{N[7*i+6]};
    end
endgenerate
endmodule

module Fadder #(parameter n) (input [n-1:0]A,B,input Ci,output [n-1:0]So,output Co);
    assign #(n*37,n*36) {Co,So} = A + B + Ci;
endmodule

```

D. Image of project and compiling:

Project - E:/Desktop/4th semster/Digital logic design/Files/HW/CA3/CA3_810198369/C

Name	Status	Type	Order	Modified
My1s_counter.sv	✓	Syst...	7	05/14/2021 11:01:37 ...
synable_1s_count...	✓	Verilog	6	05/14/2021 02:57:17 ...
ones_counter_TB...	✓	Syst...	4	05/14/2021 02:24:01 ...
ones_counter_syn...	✓	Syst...	5	05/14/2021 02:14:04 ...
Fadder_P2.sv	✓	Syst...	1	05/13/2021 04:44:28 ...
Fadder_P2_TB.sv	✓	Syst...	3	05/13/2021 04:40:50 ...
Fadder_P1_TB.sv	✓	Syst...	2	05/13/2021 03:42:18 ...
Fadder_P1.sv	✓	Syst...	0	05/13/2021 03:30:57 ...


Problem 5. Files: My1s_counter_TB.sv

A. System Verilog Description:

File: My1s_counter_TB.sv


```
`timescale 1ns/1ns
module My1s_counter127_TB();
logic signed [126:0]AA;
wire [6:0]NN;
My1s_counter127 UUT(AA,NN);
initial begin
AA = 127'd63;
#1000 AA = 127'd15;
#1000 AA = 127'd1;
#1000 AA = 127'd7;
#1000 AA = 127'd127;
#1000 AA = 127'd0;
#1000 AA[126] = 1'b1;
repeat (126) #1000 AA = AA >>> 1;
#1000 $stop;
end
endmodule
```

B. Image of project and compiling:

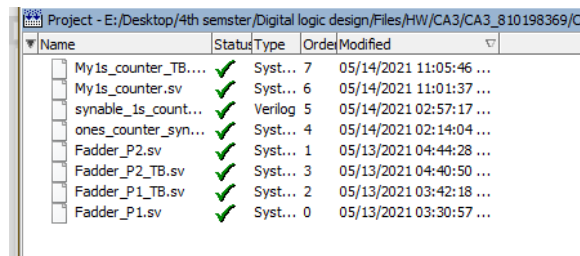

Name	Status	Type	Order	Modified
My1s_counter_TB...	✓	Syst...	7	05/14/2021 11:05:46 ...
My1s_counter.sv	✓	Syst...	6	05/14/2021 11:01:37 ...
synable_1s_count...	✓	Verilog	5	05/14/2021 02:57:17 ...
ones_counter_syn...	✓	Syst...	4	05/14/2021 02:14:04 ...
Fadder_P2.sv	✓	Syst...	1	05/13/2021 04:44:28 ...
Fadder_P2_TB.sv	✓	Syst...	3	05/13/2021 04:40:50 ...
Fadder_P1_TB.sv	✓	Syst...	2	05/13/2021 03:42:18 ...
Fadder_P1.sv	✓	Syst...	0	05/13/2021 03:30:57 ...

c. Waveform:

 

Problem 6. Files: ones_counter_synable.sv

A. System Verilog Description:


File: ones_counter_synable.sv

```
`timescale 1ns/1ns
module ones_counter_synable(input [126:0]A,output logic [6:0]N);
    int i;
    always @ (A) begin
        #777 N=7'd0;
        for (i=0;i<127;i=i+1) begin
            if (A[i] == 1'b1) N=N+1;
        end
    end
endmodule
```

Testbench: ones_counter_synable_TB.sv

```
`timescale 1ns/1ns
module ones_counter_synable_TB();
    logic signed [126:0]AA;
    wire [6:0]NN;
    ones_counter_synable UUT(AA,NN);
    initial begin
        AA = 127'd63;
        #1000 AA = 127'd15;
        #1000 AA = 127'd1;
        #1000 AA = 127'd7;
        #1000 AA = 127'd127;
        #1000 AA = 127'd0;
        #1000 AA[126] = 1'b1;
        repeat (126) #1000 AA = AA >>> 1;
        #1000 $stop;
    end
endmodule
```

B. Waveform: (Same result with problem 4)

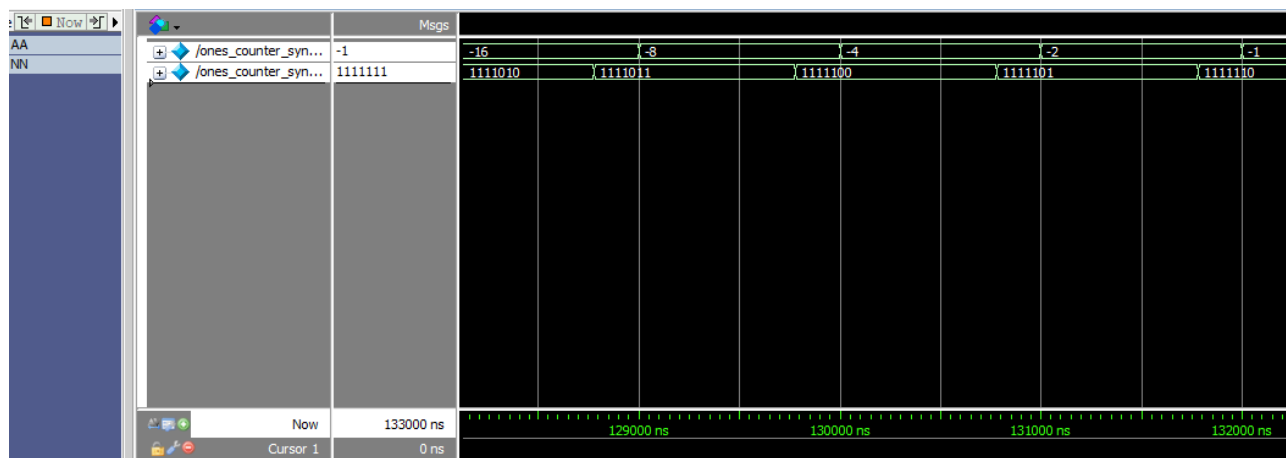

Problem 7.

Part a. Synthesizing Problem 4's module:

For this part we most make Problem 4's module as a synthesizable description. So we merge the two module used in a module and make file as Verilog description (.v) .

File: Myls_counter_P4_synable.v

```
`timescale 1ns/1ns
module Myls_counter_P4_synable(input [126:0]A,output [6:0]N);
    wire [63:0]B;
    wire [47:0]C;
    wire [31:0]D;
    wire [19:0]E;
    wire [11:0]F;
    genvar i;
    generate
        for (i=0;i<32;i=i+1) begin: Fa1bit
            assign #(1*37,1*36) {B[2*i+1],B[2*i]} = A[3*i+1] + A[3*i] + A[3*i+2];
        end
        for (i=0;i<16;i=i+1) begin: Fa2bit
            assign #(2*37,2*36) {C[3*i+2],C[3*i+1],C[3*i]} = {B[4*i+3],B[4*i+2]} +
{B[4*i+1],B[4*i]} + A[96+i];
        end
        for (i=0;i<8;i=i+1) begin: Fa3bit
            assign #(3*37,3*36) {D[4*i+3],D[4*i+2],D[4*i+1],D[4*i]} =
{C[6*i+5],C[6*i+4],C[6*i+3]} + {C[6*i+2],C[6*i+1],C[6*i]} + A[112+i];
        end
        for (i=0;i<4;i=i+1) begin: Fa4bit
            assign #(4*37,4*36) {E[5*i+4],E[5*i+3],E[5*i+2],E[5*i+1],E[5*i]} =
{D[8*i+7],D[8*i+6],D[8*i+5],D[8*i+4]} + {D[8*i+3],D[4*i+2],D[8*i+1],D[8*i]} + A[120+i];
        end
        for (i=0;i<2;i=i+1) begin: Fa5bit
            assign #(5*37,5*36) {F[6*i+5],F[6*i+4],F[6*i+3],F[6*i+2],F[6*i+1],F[6*i]} =
{E[10*i+9],E[10*i+8],E[10*i+7],E[10*i+6],E[10*i+5]} +
{E[10*i+4],E[10*i+3],E[10*i+2],E[10*i+1],E[10*i]} + A[124+i];
        end
        for (i=0;i<1;i=i+1) begin: Fa6bit
            assign #(6*37,6*36) N =
{F[12*i+11],F[12*i+10],F[12*i+9],F[12*i+8],F[12*i+7],F[12*i+6]} +
{F[12*i+5],F[12*i+4],F[12*i+3],F[12*i+2],F[12*i+1],F[12*i]} + A[126+i];
        end
    endgenerate
endmodule
```

Synthesized file of this part: **Synthesized_P4.v**

Part b. Synthesizing Problem 6's module:

For this part we most make Problem 6's module as a synthesizable description. So we make file as Verilog description (.v) .

File: ones_counter_P6_synable.v

```

`timescale 1ns/1ns
module ones_counter_synable(input [126:0]A,output reg [6:0]N);
    integer i;
    always @ (A) begin
        #777 N=7'd0;
        for (i=0;i<127;i=i+1) begin
            if (A[i] == 1'b1) N=N+1;
        end
    end
endmodule

```

```

Removed 0 unused modules.

2.23. Printing statistics.

=== ones_counter_synable ===

Number of wires:          3189
Number of wire bits:      3321
Number of public wires:   2
Number of public wire bits: 134
Number of memories:       0
Number of memory bits:    0
Number of processes:      0
Number of cells:          3194
  $_AND_                   244
  $_AOI3_                  592
  $_MUX_                   496
  $_NAND_                  134
  $_NOR_                   837
  $_NOT_                   13
  $_OAI3_                   9
  $_OR_                    9
  $_XNOR_                  620
  $_XOR_                   240

2.24. Executing CHECK pass (checking for obvious problems).
Checking module ones_counter_synable..
Found and reported 0 problems.

```

```

4.1.2. Re-integrating ABC results.
ABC RESULTS:      NAND cells:      1290
ABC RESULTS:      NOR cells:       1779
ABC RESULTS:      NOT cells:        540
ABC RESULTS:      internal signals: 3187
ABC RESULTS:      input signals:    127
ABC RESULTS:      output signals:   7
Removing temp directory.

```

Synthesized file of this part: **Synthesized_P6.v**

Result:

We have more gates and cells in synthesized of problem 4 (with for and always).