

به نام خدا



UNIVERSITY OF TEHRAN  
Electrical and Computer Engineering Department

# Computer Assignment 2

Digital Systems I - ECE 894

Deadline : 28 Farvardin 1400

**Erfan Panahi**

**810198369**

Spring 1400

# List of Problems:

## Computer Assignment 2

Problem 1.

Page 2 ([Link](#))

Problem 2.

Page 3 ([Link](#))

Problem 3.


Page 5 ([Link](#))

Problem 4.

Page 8 ([Link](#))

## Problem 1. File: MUX4to1.sv

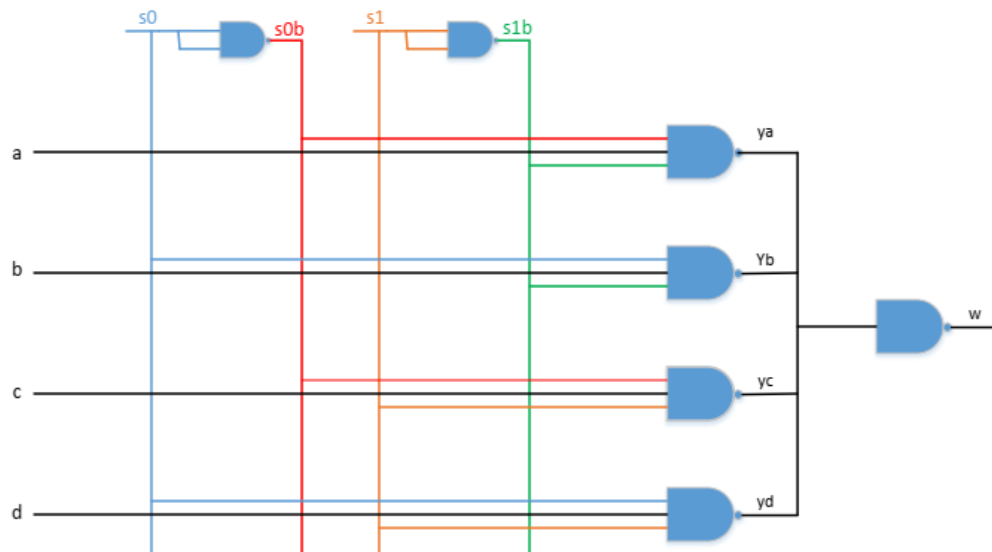- A. **Circuit diagram:** According to Part 3 of CA1, We use this Circuit to write the description of 4-to-1 MUX. (Using 'assign')



- B. **Worst-cases:** The worst cases in Part 3 of CA1 was:

**Gate-Level:**  $T_{o1} = 42\text{ns}$  ,  $T_{o0} = 39\text{ns}$

**Transistor-Level:**  $T_{o1} = 32\text{ns}$  ,  $T_{o0} = 31\text{ns}$


We use Gate-Level worst cases to write the 4-to-1 MUX module.

- c. **System Verilog Description:**

File: MUX4to1.sv


```
`timescale 1ns/1ns
module MUX4to1(input [3:0]A,[1:0]N,output w);
    assign #(42,39) w = ~ ( ~ ( A[0] & ~N[0] & ~N[1] )
        & ~ ( A[1] & N[0] & ~N[1] )
        & ~ ( A[2] & ~N[0] & N[1] )
        & ~ ( A[3] & N[0] & N[1] ) );
Endmodule
```

## D. Image of project and compiling:

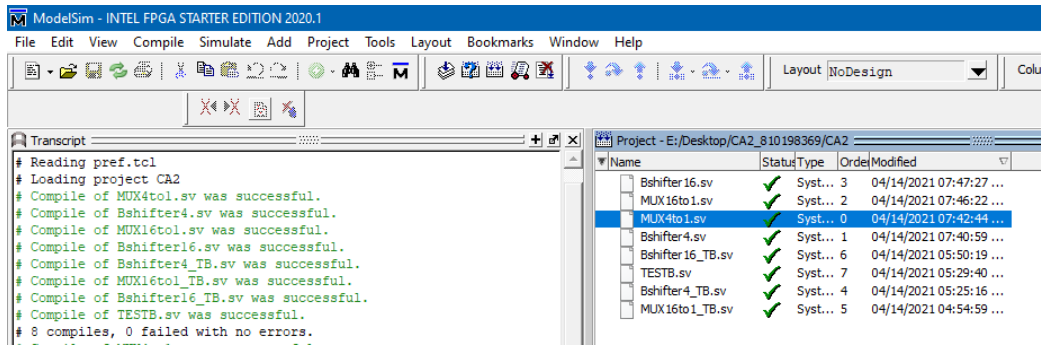

## Problem 2. Files: Bshifter4.v – Bshifter4\_TB.v
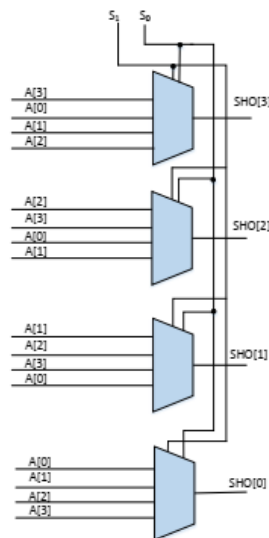
### A. Circuit diagram: The circuit for 4-bit barrel shifter is shown here:



### B. Worst-cases:

All MUXs are parallel. So we can say that the worst case happens when worst case of a MUX happens. The greatest delay of a MUX is 42 (for output=1). So the worst case for the given circuit happens when one digit of input [0:3] input is 1. We expect the worst case delay would be **42ns**.

$$A = 0101, \quad N = 00 \rightarrow N = 01$$

$$\Rightarrow \text{Delay} = T_{o1} (4 - t_o - 1 \text{ MUX}) = 42\text{ns} \text{ (worst case)}$$

### c. System Verilog Description:


#### File: Bshifter4.sv

```
`timescale 1ns/1ns
module Bshifter4(input [3:0]A,[1:0]N,output [3:0]SHO);
    MUX4to1 G1({A[2],A[1],A[0],A[3]},N,SHO[3]);
    MUX4to1 G2({A[1],A[0],A[3],A[2]},N,SHO[2]);
    MUX4to1 G3({A[0],A[3],A[2],A[1]},N,SHO[1]);
    MUX4to1 G4({A[3],A[2],A[1],A[0]},N,SHO[0]);
endmodule
```

#### File: Bshifter4\_TB.sv


```
`timescale 1ns/1ns
module Bshifter4_TB();
    logic [3:0]AA;
    logic [1:0]NN;
    wire [3:0]SSHO;
    Bshifter4 R(AA,NN,SSHO);
    initial begin
        #100 AA=4'b1010;
        #200 NN=2'b00;
        #200 NN=2'b01;
        #200 NN=2'b10;
        #200 NN=2'b11;
        #200 AA=4'b1101;
        #200 NN=2'b11;
        #200 NN=2'b10;
        #200 NN=2'b01;
        #200 NN=2'b00;
        #200 AA=4'b0001;
        #200 NN=2'b00;
        #200 NN=2'b01;
        #200 NN=2'b10;
        #200 NN=2'b11;
        #200;
    end
endmodule
```

### d. Image of project and compiling:

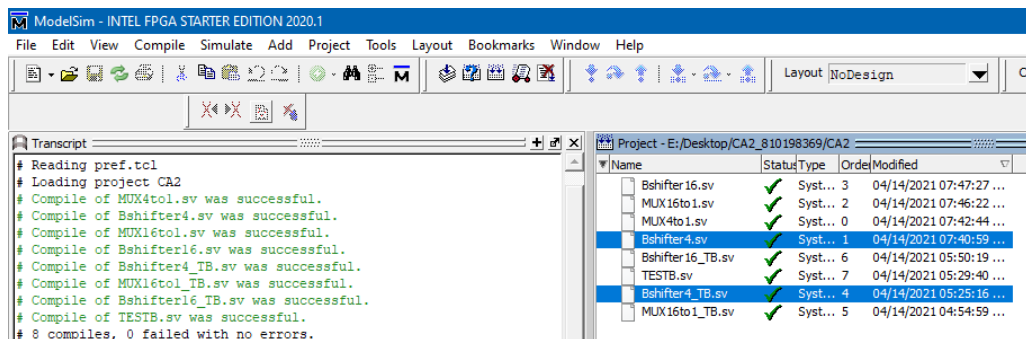

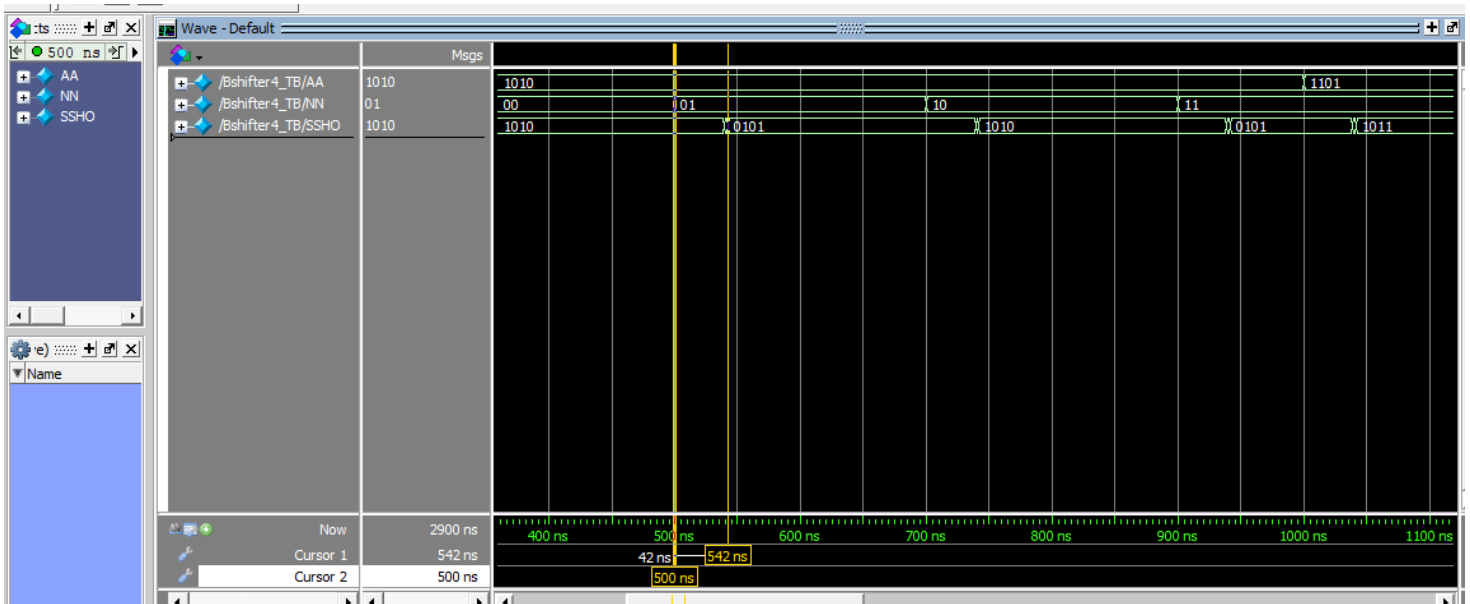
E. **Waveform:** worst case is shown on the waveform.

As expected worst case is **42ns** on the waveform:



### Problem 3. Files: MUX16to1.sv – MUX16to1\_TB.sv

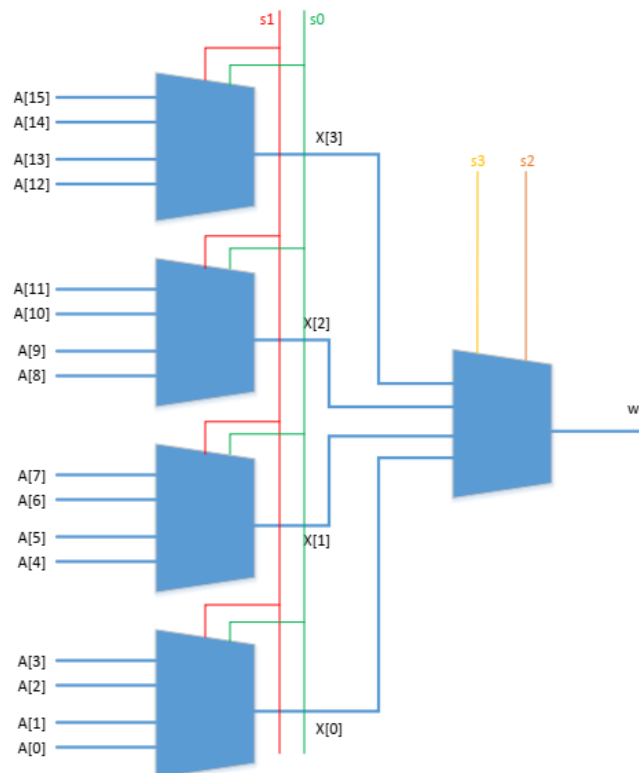A. **Circuit diagram:** The circuit for 16-to-1 MUX is shown here:



## B. Worst-cases:

### a) Worst case to 1:

Worst case to 1 happens when both MUXs (drives to 0 and) after the change drives to 1. So we expect the worst case to 1 delay would be **84ns**.

$A = 1011011110111011, \quad N = 1110 \rightarrow N = 1111$

$$\Rightarrow \text{Delay} = 2 \times T_{01} = 2 \times 42 = 84\text{ns} \text{ (worst case to 1)}$$

### b) Worst case to 0:

Worst case to 0 happens when after the change first MUX drives to 1 and the last MUX drives to 0. But actually the last MUX drives 0 sooner and delay of MUX that drives to 1 is not important. So we expect the worst case to 1 delay would be **78ns**.

$A = 1011011110111011, \quad N = 1111 \rightarrow N = 1110$

$$\Rightarrow \text{Delay} = 2 \times T_{00} = 2 \times 39 = 78\text{ns} \text{ (worst case to 0)}$$

## c. System Verilog Description:

### File: MUX16to1.sv

```
`timescale 1ns/1ns

module MUX16to1(input [15:0]A,[3:0]N,output w);
    wire [3:0]x;
    MUX4to1 g1({A[15],A[14],A[13],A[12]},{N[1],N[0]},x[3]);
    MUX4to1 g2({A[11],A[10],A[9],A[8]},{N[1],N[0]},x[2]);
    MUX4to1 g3({A[7],A[6],A[5],A[4]},{N[1],N[0]},x[1]);
    MUX4to1 g4({A[3],A[2],A[1],A[0]},{N[1],N[0]},x[0]);
    MUX4to1 g5(x,{N[3],N[2]},w);
endmodule
```

### File: MUX16to1\_TB.sv

```
`timescale 1ns/1ns
module MUX16to1_TB();
    logic [15:0]AA;
    logic [3:0]NN;
    wire ww;
    MUX16to1 R(AA,NN,ww);
```


```

initial begin
    #100 AA=16'b0101010101010101;
    #100 NN=4'd3;
    #100 NN=4'd2;
    #100 NN=4'd0;
    #100 NN=4'd1;
    #100 AA=16'b1011011110111011;
    #100 NN=4'b1111;
    #100 NN=4'b1110;
    #100 NN=4'b1111;
    #100 NN=4'b1011;
    #100 AA=16'b1011111111111111;
    #100 NN=4'b1111;
    #100 NN=4'b1110;
    #100 NN=4'b1100;
    #100 NN=4'b1110;
    #100 AA=16'd1038;
    #100 NN=4'b0000;
    #100 NN=4'b0001;
    #100 NN=4'b0011;
    #100 NN=4'b0111;
    #100 NN=4'b1111;
    #100 AA=16'd21;
    #100 NN=4'd0;
    #100 NN=4'd1;
    #100 NN=4'd2;
    #100 NN=4'd3;
    #100 NN=4'd4;
    #100 NN=4'd5;
    #100;

end
endmodule

```


#### D. Image of project and compiling:

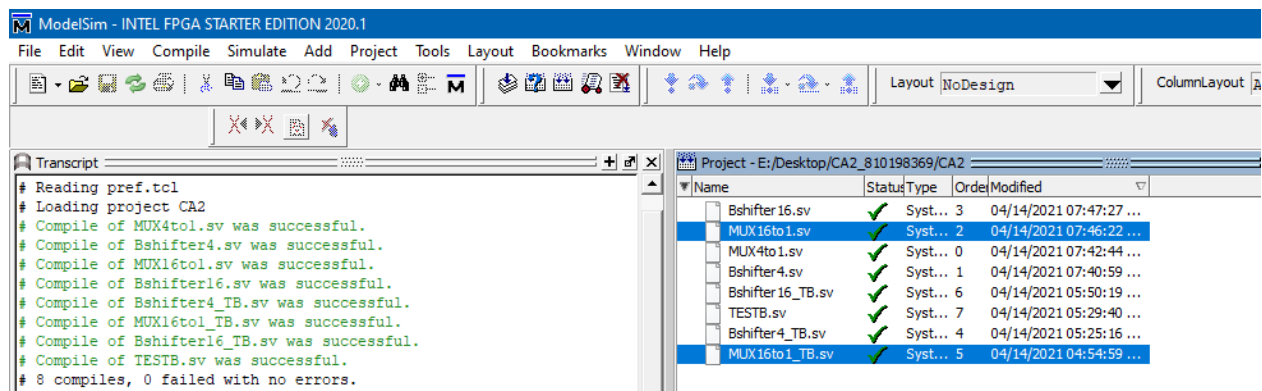




E. **Waveform:** worst case is shown on the waveform (next page).

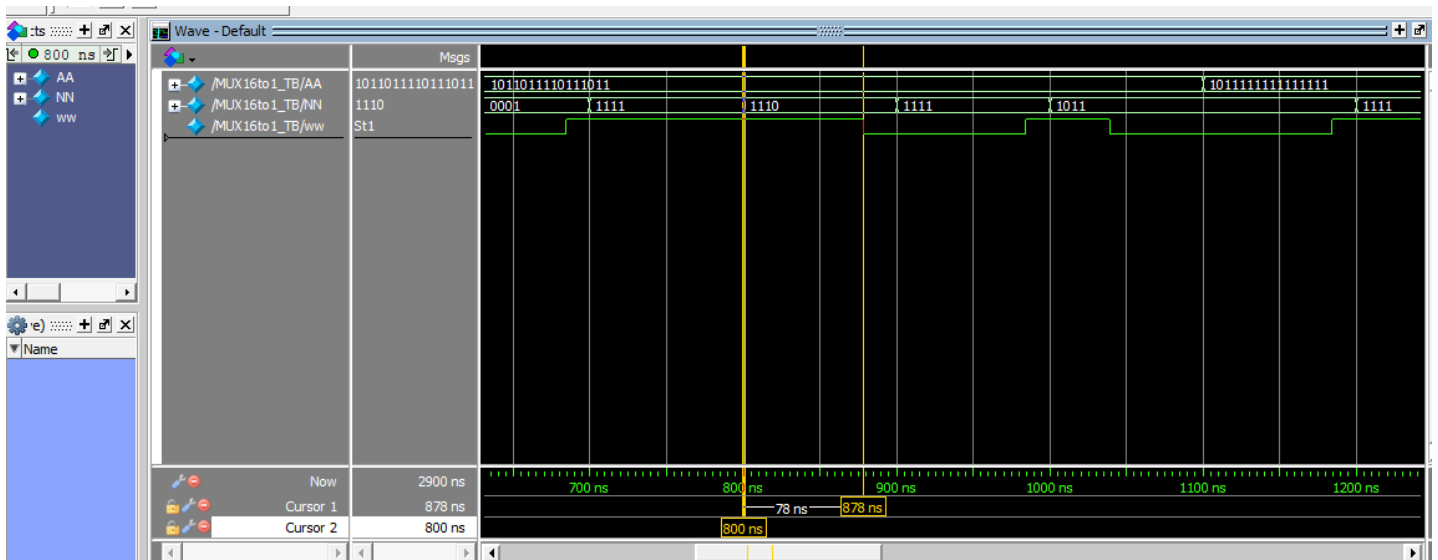a) As expected worst case to 0 is 78ns on the waveform:



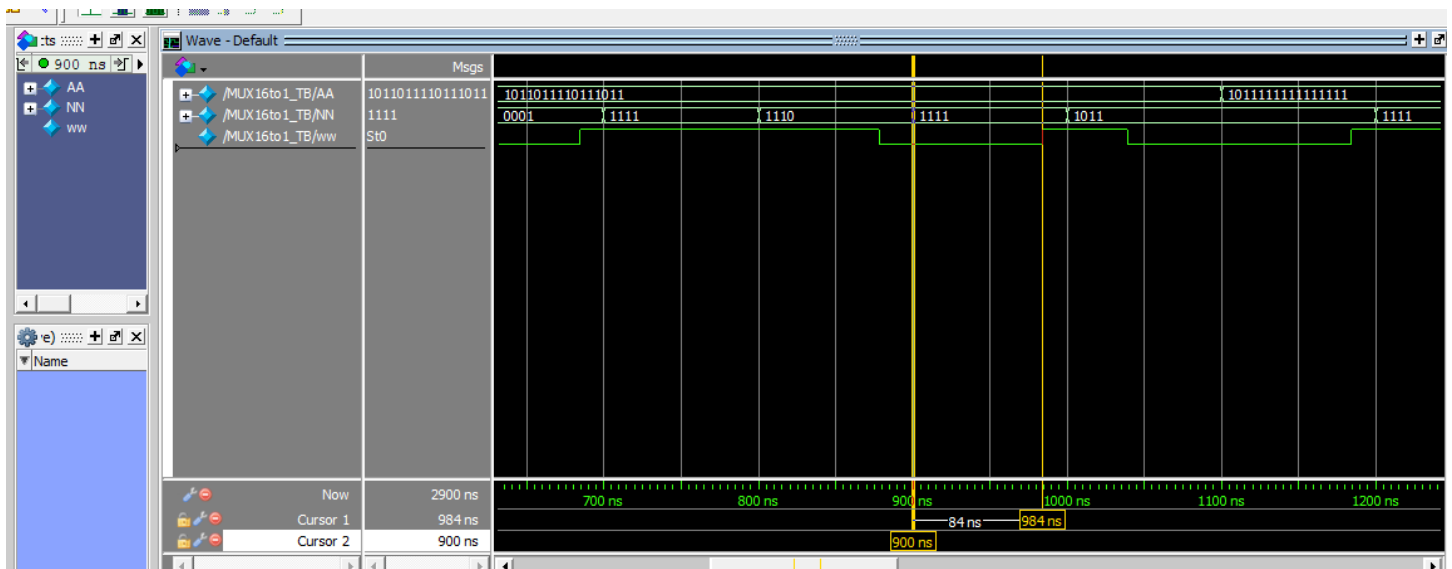
**b) As expected worst case to 1 is 84ns on the waveform:**



## Problem 4. Files: Bshifter16.sv – Bshifter16\_TB.sv

A. **Circuit diagram:** The circuit for 16-bit barrel shifter (Using 16-to-1 MUX) is shown in the next page:

(Blocks are 16-to-1 MUX)

 

## B. Worst-cases:

All MUXs are parallel. So we can say that the worst case happens when worst case of a MUX happens. The greatest delay of a MUX is 84 (worst case to 1, according to Part3). So the worst case for the given circuit happens when one digit of input [0:3] input is 1. We expect the worst case delay would be **84ns**.

$A = 0000\ 0000\ 0000\ 0001,$        $N = 0000 \rightarrow N = 0001$

$\Rightarrow \text{Delay} = \text{To1}(16 - \text{to} - 1 \text{ MUX}) = 84\text{ns (worst case)}$

## c. System Verilog Description:

### File: Bshifter16.sv

```
`timescale 1ns/1ns
module Bshifter16(input [15:0]A,[3:0]N,output [15:0]SHO);
MUX16to1 G1({A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15]},N,SHO[15]);
MUX16to1 G2({A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14]},N,SHO[14]);
MUX16to1 G3({A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13]},N,SHO[13]);
MUX16to1 G4({A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12]},N,SHO[12]);
MUX16to1 G5({A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11]},N,SHO[11]);
MUX16to1 G6({A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10]},N,SHO[10]);
MUX16to1 G7({A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9]},N,SHO[9]);
MUX16to1 G8({A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8]},N,SHO[8]);
MUX16to1 G9({A[6],A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7]},N,SHO[7]);
MUX16to1 G10({A[5],A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6]},N,SHO[6]);
MUX16to1 G11({A[4],A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5]},N,SHO[5]);
MUX16to1 G12({A[3],A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4]},N,SHO[4]);
MUX16to1 G13({A[2],A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3]},N,SHO[3]);
MUX16to1 G14({A[1],A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2]},N,SHO[2]);
MUX16to1 G15({A[0],A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1]},N,SHO[1]);
MUX16to1 G16({A[15],A[14],A[13],A[12],A[11],A[10],A[9],A[8],A[7],A[6],A[5],A[4],A[3],A[2],A[1],A[0]},N,SHO[0]);
endmodule
```

### File: Bshifter16\_TB.sv

```
`timescale 1ns/1ns
module Bshifter16_TB();
    logic [15:0]AA;
    logic [3:0]NN;
    wire [15:0]SSHO;
    Bshifter16 R(AA,NN,SSHO);
    initial begin
        AA=16'b0000000000000001;
        #100 NN=4'b0000;
        #100 NN=4'b0001;
        #100 NN=4'b0011;
        #100 NN=4'b0111;
        #100 NN=4'b1111;
        #100 AA=16'b0101010101010101;
        #100 NN=4'd3;
    end
endmodule
```


```

#100 NN=4'd2;
#100 NN=4'd0;
#100 NN=4'd1;
#100 AA=16'b1011011110111011;
#100 NN=4'b1111;
#100 NN=4'b1110;
#100 NN=4'b1111;
#100 NN=4'b1011;
#100 AA=16'b1011111111111111;
#100 NN=4'b1111;
#100 NN=4'b1110;
#100 NN=4'b1100;
#100 NN=4'b1110;
#100 AA=16'd1038;
#100 NN=4'b0000;
#100 NN=4'b0001;
#100 NN=4'b0011;
#100 NN=4'b0111;
#100 NN=4'b1111;
#100 AA=16'd21;
#100 NN=4'd0;
#100 NN=4'd1;
#100 NN=4'd2;
#100 NN=4'd3;
#100 NN=4'd4;
#100 NN=4'd5;
#100;
#1000;

end
endmodule

```

#### D. Image of project and compiling:

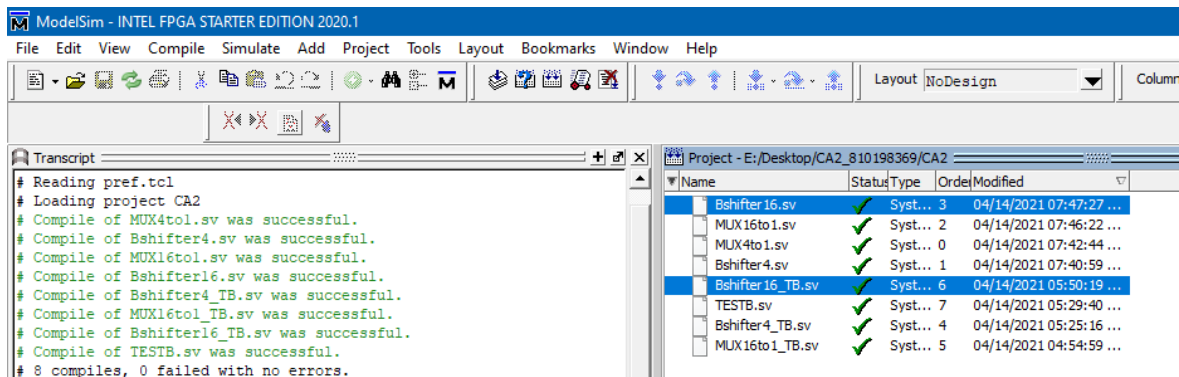

#### A. Waveform: worst case is shown on the waveform (next page).

As expected worst case is **84ns** on the waveform:

